

## General formulae

## ① Ohm's law

$$V = IR \quad ; \quad V/I = R \quad , \quad V/R = I$$

## ② Power

$$P = VI = I^2 R = \frac{V^2}{R}$$

## ③ Energy

$$E = P \times t = VIt$$

## ④ Res. in series

for same  $I$ , diff  $V$

$$E = V_1 + V_2 + \dots$$

$$= R_1 I + R_2 I + \dots$$

$$E = (R_{eq}) I$$

## ⑤ Voltage division rule

$$I = \frac{E}{R_1 + R_2}$$

$$\therefore V_1 = \frac{R_1}{R_1 + R_2} E \quad ; \quad V_2 = \frac{R_2}{R_1 + R_2} E$$

## ⑥ Res in parallel

for same  $V$ , diff  $I$

$$I = I_1 + I_2 + \dots$$

$$= \frac{E}{R_1} + \frac{E}{R_2}$$

$$I = \frac{E}{R_{eq}}$$

[  $V = E =$  same & not different ]


## ⑦ Current division rule

$$E = \left( \frac{R_1 R_2}{R_1 + R_2} \right)^{R_{eq}} I$$

$$\therefore \underbrace{I_1}_{\frac{E}{R_1}} = \frac{R_2}{R_1 + R_2} I \quad ; \quad I_2 = \frac{R_1}{R_1 + R_2} I \quad \equiv \quad \frac{I R_{eq}}{R + R_{eq}}$$

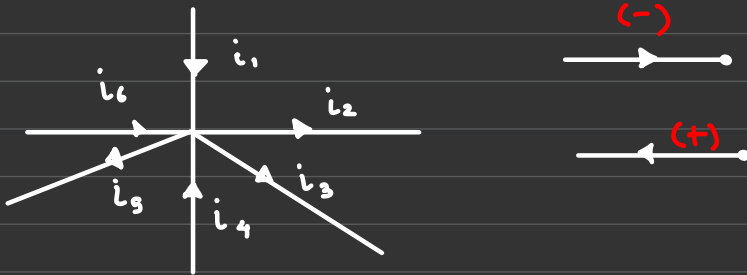
## ⑧ KCL

The algebraic sum of all currents through a junction is zero


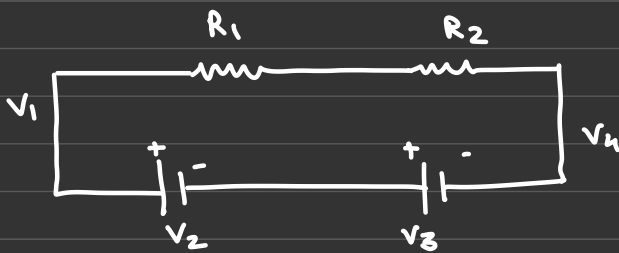
## ⑨ KVL

The algebraic sum of elements voltages around a closed loop is zero




$$V_1 - V_2 - V_3 + V_4 = 0$$

## • Network theorems


### ① Thevenin's theorem

Converts complex network to simple circuits

Steps :-

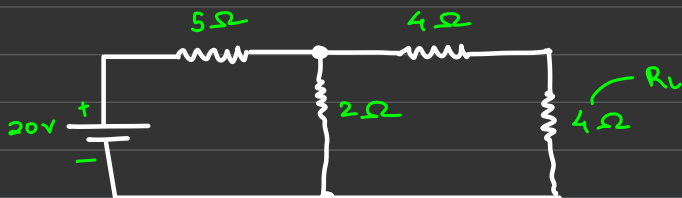

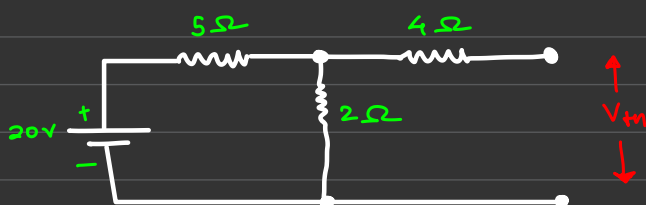1. Disconnect the load resistance and make its terminals open



2. find  $V_{th}$

$$\rightarrow R_{eq} = 5 + 2 = 7 \Omega \quad (4 \Omega \text{ is } \infty)$$

$$I = 20 / 7 = 2.8 \text{ A}$$

$$\text{Now, } V_{th} = V_{2\Omega} = 2.8 \times 2 = 5.7 \text{ V}$$

3. find  $R_{th}$  by SC the Voltage source and OC current source



$$R_{th} = (5 \parallel 2) + 4 = 5.4 \Omega$$

4. Draw the thevenin eq. circuit and place the disconnected  $R_L$  at the same place



5. find current through  $R_L$

$$I_L = \frac{I R_{th}}{R_L + R_{th}} = \frac{V_{th}}{R_{th} + R_L}$$

$$= \frac{5.7}{5.8 + 4} = 0.6 \text{ A}$$

### ③ Maximum Power transfer theorem

max P transfer from source to load occurs when  $R_L = R_{th}$

Steps :-




1. first 3 steps same as thevenin's thm

$$V_{th} = 30 \text{ volts}$$

$$R_{th} = 2.1 \Omega$$

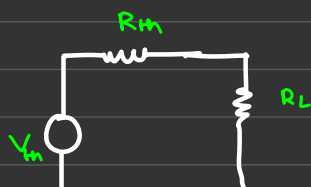4. Reconnect  $R_L$  and draw thevenin's eq



here

$$R_L = R_{th} = 2.1 \Omega \quad (\text{MPT})$$

5. find  $I_L$  and  $P_{max}$


$$I_L = \frac{V_{th}}{R_L + R_{th}} = \frac{V_{th}}{2R}$$

$$P_{max} = \frac{V_{th}^2}{2(2R)} = \frac{V^2}{4R}$$


### ② Superposition theorem

$I$  or  $V$  in any element is equal to the algebraic sum of current or voltage that would have been produced by individual circuits

Steps :-

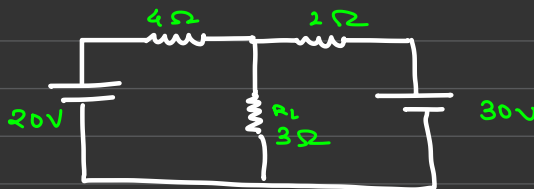

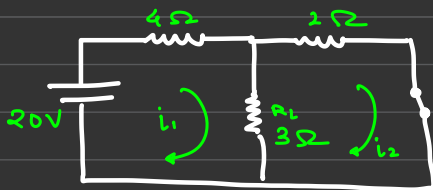1. Consider any 1 source of  $V$  or  $I$ , replace other sources by  $sc$  /  $oc$



## • AC Circuits

- i) Basic terms
- ii) Average value
- iii) RMS
- iv) Single phase
- v) Analysis
- vi) Three-phase

## • Basic terms

**3. Periodic Waveform** Periodic waveform is one which repeats itself after definite time intervals.

### 4. Sinusoidal and Non-Sinusoidal Waveform

**Sinusoidal waveform** It is an alternating waveform in which sine law is followed.

**Non-sinusoidal waveform** It is an alternating waveform in which sine law is not followed.

**5. Cycle** One complete set of positive and negative halves constitute a cycle.


**6. Amplitude** The maximum positive or negative value of an alternating quantity is called the amplitude.

**7. Frequency** The number of cycles per second of an alternating quantity is known as frequency. Unit for frequency is expressed as c/s or Hertz (Hz).

**8. Period (T)** Time period of an alternating quantity is the time taken to complete one cycle. Time period is equal to the reciprocal of frequency. Time period is expressed in secs.

**9. Phase** The phase at any point on a given wave is the time that has elapsed since the quantity has last passed through zero point of reference and passed positively.

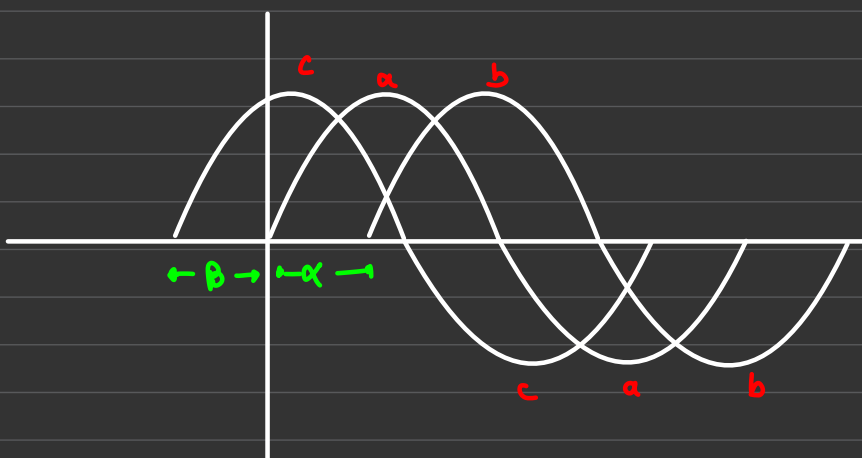**10. Phase Difference** The term is used to compare the phase of two waveforms or alternating quantities.




$$e_A = E_m \sin \omega t$$

$$e_B = E_m \sin(\omega t + \beta) \text{ (leads)}$$

$$e_C = E_m \sin(\omega t - \alpha) \text{ (lags)}$$

- Avg Value

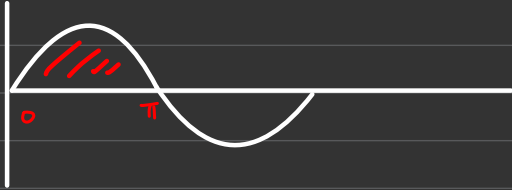The steady current that is transferred across a circuit the same charge as AC in same time



$$\begin{aligned} I_{av} &= \int_0^{\pi} \frac{i \cdot d\theta}{2\pi} \\ &= \int_0^{\pi} \frac{I_m \sin\theta \cdot d\theta}{\pi} \\ &= \frac{I_m}{\pi} [-\cos\theta]_0^{\pi} \\ &= \frac{2I_m}{\pi} \end{aligned}$$

$$I_{av} = 0.637 I_m$$

- RMS Value

$$\sqrt{i^2}$$

rest ppt