

- Topics

PN - Junc

BJT

JFET

MOSFET

IGBT

SCR

Power Conv

SMPs

KMAP



- BJT

Bipolar Junction Transistor is a three terminal semiconductor device. Depends on both majority and minority carriers

Used as amplifier & oscillator in circuits.

- Transistor biasing

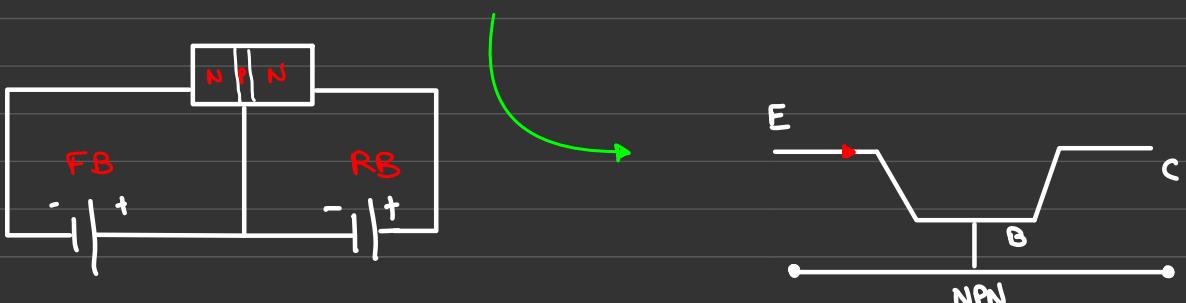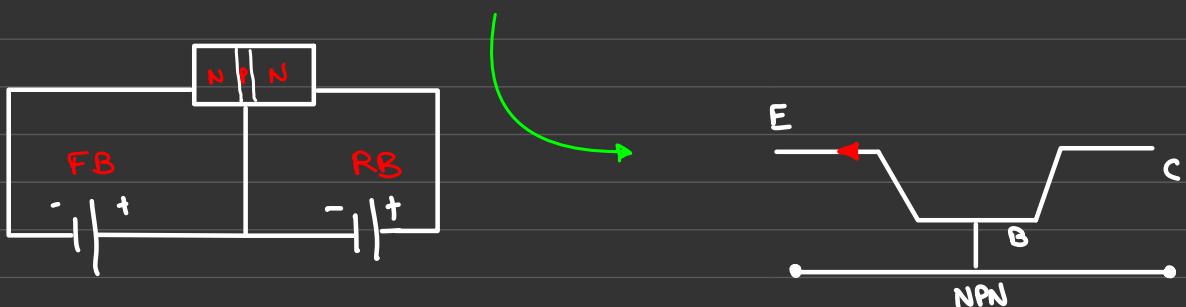Emitter-base junction is forward biased & Collected base junction is reverse biased. IE flows to the base then into the collector




① NPN Transistor

When forward biasing is applied to the emitter-base junction, it causes a lot of e⁻s from the emitter region to crossover to the base region.

The base region size is very small & hence very less number of e⁻ combine with holes.

The majority e⁻ then crossover to the collector region constituting a collector current.

Summed to give $I_E = I_C + I_B$

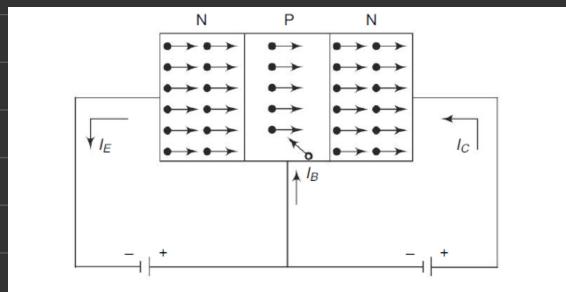


② PNP Transistor

When FB applied to E-B junc, holes from emitter region to crossover to the base region (slightly doped N-type imp)

No of e⁻ in base is less, hence only few combine and make I_B , rest go to collector region & make I_C

$\therefore I_E = I_C + I_B$

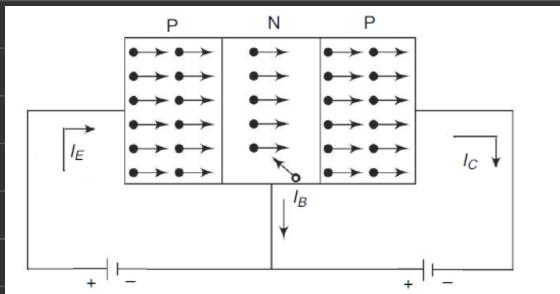

- FET

A device in which flow of current thru conducting region is controlled by elec. fld

A unipolar device



- N-channel JFET

Made of N-type bar made of silicon

Construction : i) Source (S) : Connected to -ve of the battery
e⁻ are maj cars. they enter here


ii) Drain (D) : Connected to +ve pole of the bat
maj cars leave from here

iii) Gate (G) : Both terminals joined here
Heavy doped P-type Si diffused on both sides

Operation :-

Case - 1 : $V_{GS} = 0 \neq V_{DS} = 0$

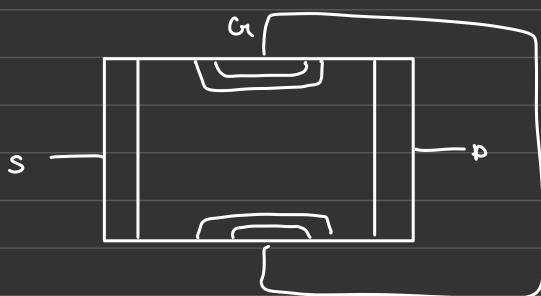- No Volt b/w D, S, G
- Thickness of dep region is uniform




Case - 2 : $V_{DS} = 0$, $V_{GS} < 0$

- PN junc RB
- As V_{GS} dec frm 0, rev Vol inc.
- The thickness of dep reg inc until two meet
- The channel cutoff at Volt V_C


Case - 3 : $V_{GS} = 0$, $V_{DS} > 0$

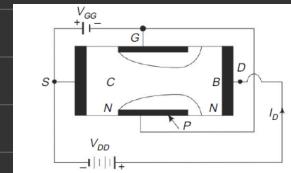- Drain is +ve
- maj curr (e^- s) flow frm S \rightarrow D with I_D ($D \rightarrow S$)
- Becoz R and V_{DS} , -ve pot inc ($S \rightarrow D$)
- \therefore rev volt also inc, hence thick inc in wedge shape
- as $V_{DS} \uparrow$, cross-sectional area \downarrow
- When becomes min, it called V_p (pinch off voltage)



Case - 4 : $V_{GS} < 0$, $V_{DS} > 0$

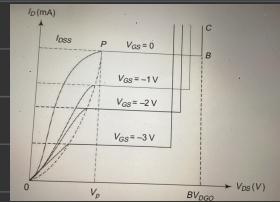- When G_S is ($-V_C$), rev volt \uparrow
- \therefore same plot for $V_{GS} = 0$



JFET vs BJT

JFET

- Only operates on maj curr
- less noisy
- High impedance ($> 100 M\Omega$)
- less sensitive to temp
- easy to fabricate
- less Volt, high signal distortion

BJT

- Operates on both maj & min curr
- more noisy
- less compared
- more
- hard

• MOSFET

It's a common term of Insulated Gate Field Effect Transistor





Principle: By applying transverse electric field across an insulator depositing on semi mat, the thickness / R can be controlled

Construction:

- Two highly doped N^+ diffused in lightly doped substrate
- One N^+ region called S & other D
- A thin SiO_2 insulating layer on surface
- The metal area, SiO_2 layer form a parallel plate capacitor
- This is called insulated gate FET

Operation:

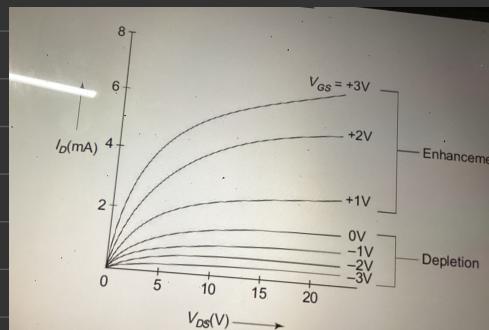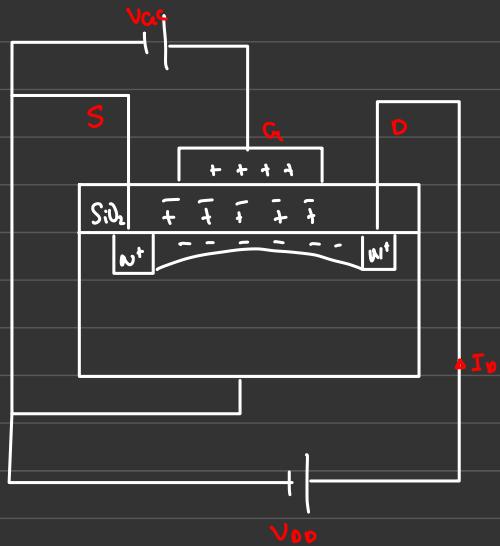- If substrate grounded & +ve voltage applied at gate
- The +ve on G induces eq (-ve) charge b/w S & D
- Thus, elec fld prod b/w S & D
- dirctn is \perp to plates of oxide
- The -ve charge on e's (min cars) in P-type form an inversion layer
- As (+ve) Volt at G inc, induced (-ve) charge in semi inc.
- Hence cond i & I flows ($S \rightarrow D$)





• Insulated Gate Transistor (IGBT)

- Has high input impedance of a MOSFET & low on-state power loss in a BJT
- P⁺ layer at drain is called collector
- When gate is +ve w.r.t emitter & gate-emitter volt > threshold voltage, n-channel formed in the p-region
- N⁻ channel short circuit n⁻ with n⁺ emitter region causing e⁻ movement in n-channel, eventually forward I_{est}.
- Three layers : P⁺ n⁻, P (PNP Trans)

$$P^+ \rightarrow E, n^- \rightarrow B, P \rightarrow C$$

if n⁻, P, n⁺ (NPN trans)
 $n^- \rightarrow C$
- Output Char : plot of I_c vs V_{ce}
(VI same as BJT)
- Transfer Char : plot I_c vs V_{ge}
 similar to MOSFET
 when V_{ge} < V_{thres}, V_{ge} \rightarrow IGBT is off-state

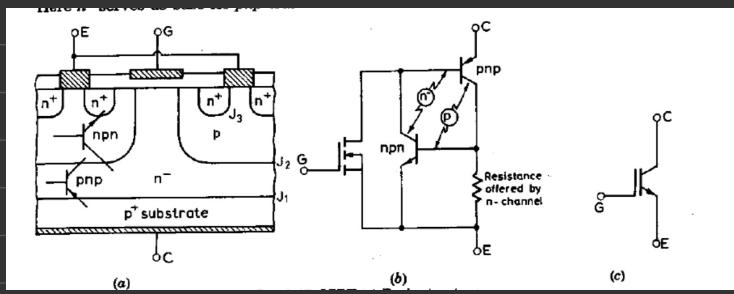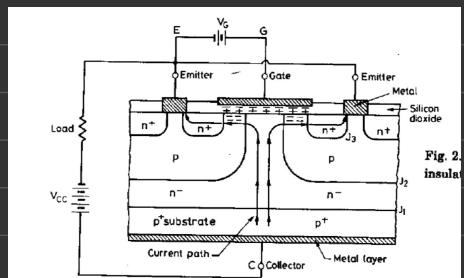
App : DC & AC motor drives, UPS
 more efficient due to small size



• Silicon Controlled Rectifier (SCR)

- four-layer, 3-terminal device
- end P-layer act as Anode
N Cathode
- Acts as a switch when FB
- When $I_C = 0$, SCR similar to PNPN diode
 $I_G < 0$, RB at $I_Z \uparrow$, V_{BR} (Breakdown V) ↑
 $I_G > 0$, RB at $I_Z \downarrow$, $V_{BR} \downarrow$
- With large +ve I_A , breakdown may occur at low volt so char of SCR similar to PN
- As SCR switched off, it can be controlled by I_A , commonly called controlled switch

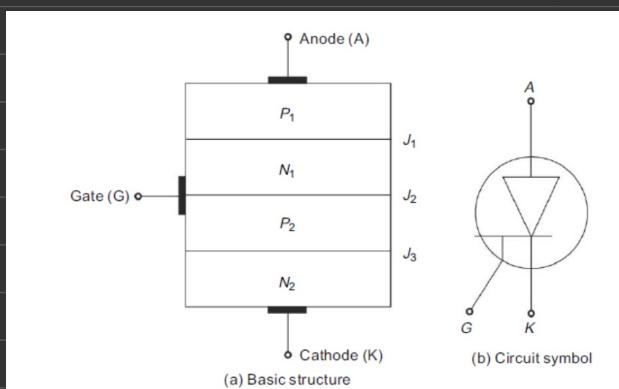
Apps: Used in relay control, motor control, inverter, battery charges



• SMPS (Switched Mode Power Supply)

- Used to obtain regulated DC output by Semicon switching methods
- highly efficient : power consumption & , heat dissipation &
- Includes switching trans (power MOSFET)
DC signal goes thru chopping (switching)
- When trans is switched on \rightarrow fully conducts curr
 $\text{off} \rightarrow$ completely blocks flow of curr
- Operates at high freq \rightarrow size & , weigh &

Working:

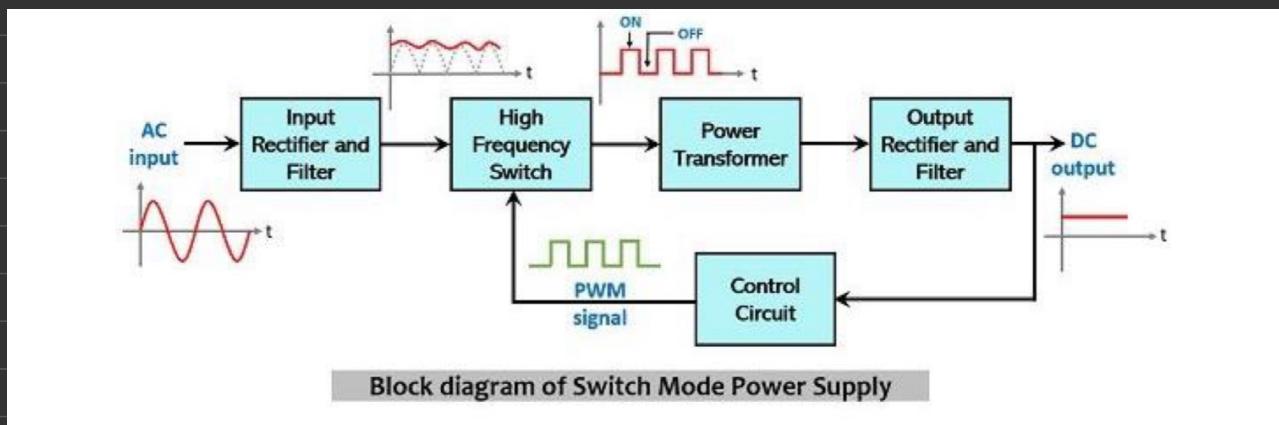

i) unregulated ac sig $\xrightarrow{\substack{\text{input} \\ \text{rect}}}$ dc signal
frm source

ii) Power transformer acts as a high freq switch,
here DC signal undergoes chopping (switching)

iii) high volt sig $\xrightarrow{\substack{\text{Power Transformer} \\ \text{step + trans}}}$ low volt level

iv) Output rect removes unwanted sig , providing a regulated signal

v) Compares obtained DC volt w reference value
DC output $>$ ref value \rightarrow chopping freq ↑ , DC volt ↑
DC output $<$ ref value \rightarrow

Adv : i) highly efficient ; 60% - 95%
ii) small size / less bulky

DisAdv : i) complex circuit
ii) volt regulation tricky
iii) prop filtration for noise

Apps : used in motor drives, security system, television sets.

• Power Convertors

1) AC → DC

i) Diode Rect :-

- ac input volt → fixed dc voltage
- single-phase / 3-phase ac sig at input
- Used in electrochem processes like electroplating

ii) Phase Controlled rectifiers

- fixed ac → variable dc
- 1/3 phase ac
- line voltage operates the rect
- Used in dc drives, compensator

2) DC → DC

i) Chopper :-

- fixed dc → variable dc
- output dc has diff ampli, controlled by low power sig
- used in SMPS, trolley trucks
- MOSFET used for fabrication

3) DC → AC

i) Inverter :-

- fixed dc → ac volt. of variable freq
- MOSFET, IGBT, etc used for fabrication
- used in induction heating supplies
- * • Thyristor : used in high power apps

4) AC → AC

i) Cycloconverters

- fixed ac → variable ac
- input freq < output freq
- used in ac motor drives

ii) AC voltage regu

- fixed ac → var ac
- same input/out freq
- two thyristors used in 11°1
- used in lightning control

• Convertors

$AC \rightarrow DC$

Diode Rec

Phase Cont Rec

$DC \rightarrow DC \rightarrow DC$ input \rightarrow DC Chopper \rightarrow Variable AC output

$DC \rightarrow AC \rightarrow$ (Inverter)

$AC \rightarrow AC$

Cycloconverter (Fixed to Variable)

AC Volt regu

• Commutation

Natural Forced

process of turning off a conducting thyristor

$i_{anode} = 0$

forcing circuit (east)
 $i_{tw} \rightarrow 0$

• logic gates

AND



$$Y = AB$$

NAND



$$Y = \overline{AB}$$

OR



$$Y = A + B$$

NOR



$$Y = A + B$$



eg implement logical expression using logic gates

$$F = ABC + ABC^I + A^I BC^I$$

$\begin{matrix} \circ & \circ & \circ \\ \bar{A} & B & C \end{matrix}$